

## \* SPPU Assignment :- A-2

### ★ Universal Shift Register (USR) (4-bit)

⇒ SR (Shift Register) is a system which shifts bits from L→R or R→L

⇒ SR can accept i/p bits in a Serial / Parallel Fashion

\* Hence we have 2 options

- Serial-In (SI)
- Parallel-In (PI)

⇒ SR can output the stored bits in a Serial/Parallel Fashion

\* Hence we have 2 options

- Serial-out (SO)
- Parallel-out (PO)

⇒ A SR which allows all combinations of above 4 options is called as USR

⇒ Thus USR has 4 operating modes:-

- i) SISO
- ii) SIPO
- iii) PISO
- iv) PIPO

⇒ USR is basically a Register ie Memory

⇒ Being a Memory it has the following aspects:-

⇒ It has a Master-Reset (Asynchronous) (Independent of clock)

⇒ It is Clock-Driven

⇒ It has Mode-select


2-bit

⇒ Based on All of the above facts, BD, FT of USR can be :-

#### Power Hierarchy :-




I/p signals	Power-Level
rst	①
clk	②

 

rst	①
clk	②
mode	③
Sin, Pin	④

 Tells us the order in which to check status of i/p signals



\* The above 4 operations will happen subject to :-

①  $rst = 0$

② At the arrival of  $\downarrow$  of clk.

\* For  $rst = 1$  :

$Sout = 0$


$Pout = 0000$

\* Mode Latency = No. of clock cycles needed to execute the Mode

\* Mode-Latency of Each Mode:-


MODE	Latency (No. of clock cycles needed)
① SISO	$4(SI) + 4(SO) = 8 \downarrow$
② SIPO	$4(SI) + 1(PO) = 5 \downarrow$
③ PISO	$1(PI) + 4(SO) = 5 \downarrow$
④ PIPO	$1(PI) + 1(PO) = 2 \downarrow$

We define clock-period = 10 ns

 

↔  
3 7

⊛ How to check status of clock?

 

⊛ Checking the Arrival of Falling-edge:-

① IF (CLK'EVENT AND CLK = '0') THEN

② IF falling-edge(CLK) THEN

⊛ Checking the Arrival of Rising-edge:-

① IF (CLK'EVENT AND CLK = '1') THEN

② IF rising-edge(CLK) THEN

⊛ Writing PROCESS for mode in TVM :-

mode : PROCESS  
BEGIN

mode <= "00";  
WAIT FOR 80 ns;

mode <= "01";  
WAIT FOR 50 ns;

mode <= "10";  
WAIT FOR 50 ns;

mode <= "11";  
WAIT FOR 20 ns;

END PROCESS;